

# CURRENT AND RESISTANCE

42


$$V = iR$$

$$E = j\rho$$


$$P = Vi = i^2 R = V^2/R$$

1. IN TERMS OF CURRENT DENSITY  $j$  [AMPS/ $m^2$ ] AND THE GEOMETRICAL MEASUREMENTS, FIND A FORMULA FOR THE CURRENT  $i$  [AMPS].

A) SEMI-CYLINDER

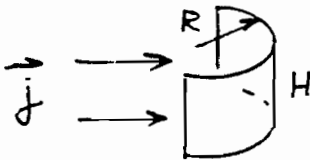


B) HEMISPHERE

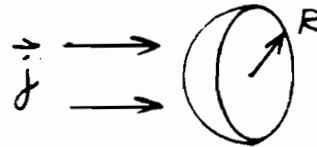

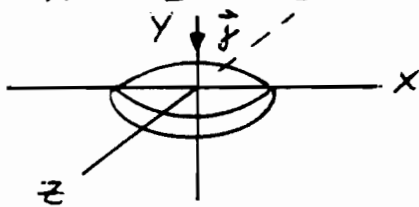C) SEMI-ELLIPSOID

$$\frac{x^2}{A^2} + \frac{y^2}{B^2} + \frac{z^2}{C^2} = 1$$



D) FLAT PLATE OF AREA "A" HIT AT A GLANCING ANGLE.



2. A CABLE, WHOSE CROSS-SECTIONAL AREA IS  $.0012 m^2$ , CARRIES A CURRENT OF 42 AMPS. FIND ITS CURRENT DENSITY.

3. AN IRON WIRE HAS CURRENT DENSITY OF  $4.8 \times 10^6 A/m^2$ .

EACH IRON ATOM CONTRIBUTES TWO VALENCE ELECTRONS TO THE "SEA OF ELECTRONS," WHICH CONSTITUTES THE CURRENT. IRON, WHOSE ATOMIC MASS IS  $56 g/mole$ , HAS A DENSITY OF  $7.9 g/cm^3$ . FIND THE DRIFT VELOCITY OF THE ELECTRONS.

4. A STEEL TROLLEY RAIL, WHOSE CROSS-SECTIONAL AREA IS  $45 cm^2$ , HAS A RESISTIVITY OF  $1.8 \times 10^{-7} \Omega \cdot m$ . FIND THE TOTAL RESISTANCE OF A TRACK  $12.5 km$  LONG.

5. SILVER HAS A RESISTIVITY OF  $1.6 \times 10^{-8} \Omega \cdot m$ . FIND ITS CONDUCTIVITY.

ANSWERS:  $i = 2RHj$     $i = -\pi R^2 j$     $i = \pi ACj$     $i = Aj \cos \theta$   
 $35000 A/m^2$     $.177 mm/sec$     $.5 \Omega$     $6.25 \times 10^7 S$

6. TUNGSTEN HAS A TEMPERATURE COEFFICIENT OF RESISTIVITY OF  $4.5 \times 10^{-3} / ^\circ\text{C}$ . AT  $25^\circ\text{C}$ , THE TUNGSTEN ELEMENT IN A TOASTER HAS A RESISTANCE OF  $30 \Omega$ . WHEN THE TOASTER IS DOING EXACTLY THAT TO THE BREAD, THE ELEMENT'S TEMPERATURE IS  $625^\circ\text{C}$ . FIND THE RESISTANCE OF THE ELEMENT AT THIS HIGHER TEMPERATURE. ( $111 \Omega$ )


7. ON THE SURFACE OF THE EARTH, AT  $20^\circ\text{C}$ , A CARBON RESISTOR HAS A VALUE OF  $160 \Omega$ . THE RESISTOR, WHOSE TEMPERATURE COEFFICIENT OF RESISTIVITY IS  $-5 \times 10^{-4} / ^\circ\text{C}$ , IS LOWER TO THE BOTTOM OF AN OIL WELL WHERE ITS RESISTANCE IS  $154 \Omega$ . FIND THE:

- A) CHANGE IN TEMPERATURE ( $75^\circ\text{C}$ )
- B) TEMPERATURE AT THE BOTTOM OF THE WELL. ( $95^\circ\text{C}$ )

8. TWO WIRES HAVE THE SAME RESISTANCE AND THE SAME CROSS SECTIONAL AREA. HOWEVER, THEY HAVE BOTH DIFFERENT LENGTHS AND DIFFERENT RESISTIVITIES. FIND A FORMULA FOR  $L_2$  IN TERMS OF  $L_1$ ,  $\rho_1$  AND  $\rho_2$ , WHERE  $L$  IS LENGTH AND  $\rho$  IS RESISTIVITY.

9. FIND A FORMULA FOR THE RESISTANCE, "R", OF A WIRE IN TERMS OF ITS RESISTIVITY " $\rho$ ", ITS MASS "m", ITS DENSITY "D" AND THE RADIUS, "r", OF ITS CROSS SECTION.

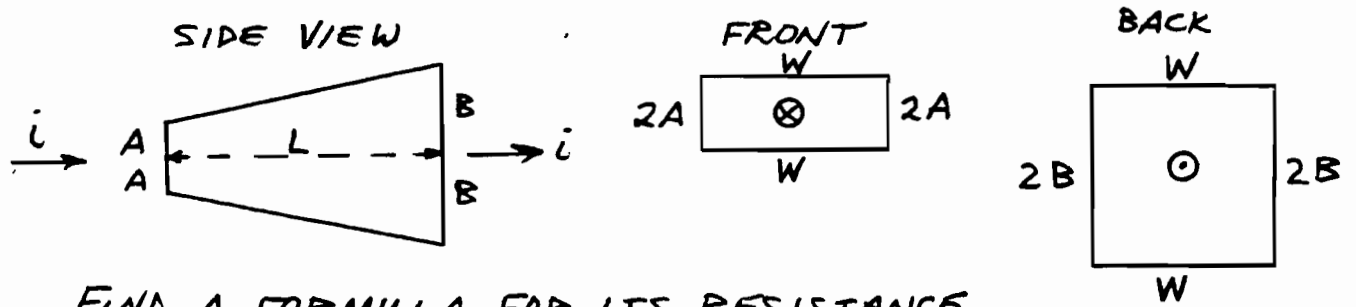10. A TRUNCATED WEDGE, WITH RESISTIVITY  $\rho$ , HAS THE DIMENSIONS SHOWN BELOW.



FIND A FORMULA FOR ITS RESISTANCE, IN TERMS OF  $L$ ,  $W$ ,  $A$ ,  $B$  AND  $\rho$ .

ANSWERS: PROBLEM 8  $L_2 = \frac{\rho_1 L_1}{\rho_2}$     9.  $R = \frac{\rho m}{\pi^2 r^2 D}$     10.  $R = \frac{\rho L}{2W(B-A)} \ln\left(\frac{B}{A}\right)$

11. A TRANSMISSION LINE BETWEEN A POWER STATION AND A FACTORY HAS A RESISTANCE OF  $.15 \Omega$  IN EACH OF THE TWO WIRES.

A) A CURRENT OF 200 A IS DELIVERED TO THE FACTORY AT 110 VOLTS. FIND:

- i) POWER DELIVERED TO THE FACTORY (22,000 W)
- ii) POWER WASTED TO HEAT BOTH WIRES (12,000 W)
- iii) TOTAL POWER GENERATED BY SAN ONOFRE (34,000 W)
- iv) PERCENT OF TOTAL POWER WASTED. (35.3%)

B) A CURRENT OF 2 AMP IS DELIVERED TO THE FACTORY AT 11,000 VOLTS. FIND:





- i) POWER DELIVERED TO FACTORY (22,000 W)
- ii) POWER WASTED TO HEAT BOTH WIRES (1.2 W)
- iii) TOTAL POWER GENERATED BY SAN ONOFRE (22,001.2)
- iv) PERCENT OF TOTAL POWER WASTED. (.00545%)

MORAL OF THE STORY: TRANSPORT ELECTRICAL ENERGY AT VERY HIGH VOLTAGE AND CONSEQUENTLY, VERY LOW CURRENT.

CIRCUITS: OHM ON THE RANGE — WHERE THE SKIES ARE UNCLOUDY ALL DAY

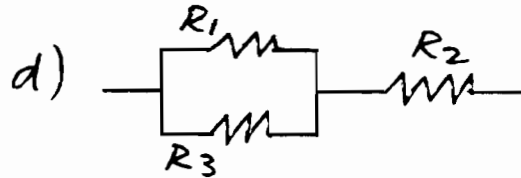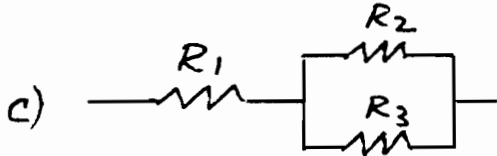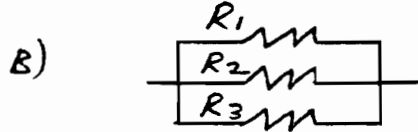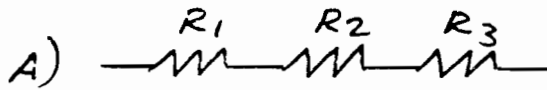1. FIND THE EQUIVALENT RESISTANCE FOR EACH OF THE FOLLOWING COMBINATIONS WHERE :




$R_1 = 132 \Omega$      $R_2 = 15 \Omega$      $R_3 = 60 \Omega$



(  $207 \Omega$ ,  $11 \Omega$ ,  $144 \Omega$ ,  $56.25 \Omega$  )

2. FOR EACH CIRCUIT, FIND :

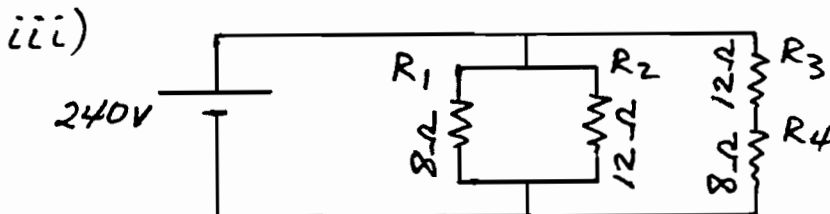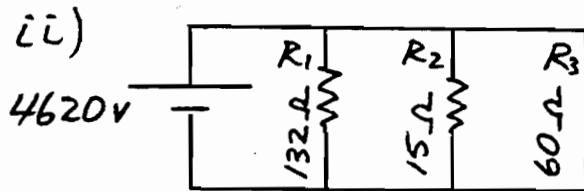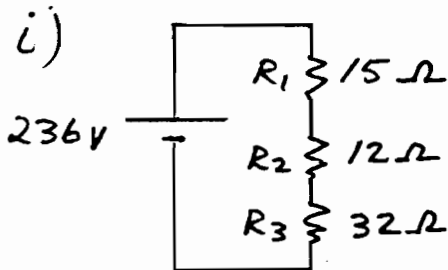- A) CURRENT FLOWING THROUGH EACH RESISTOR
- B) VOLTAGE DROP ACROSS EACH RESISTOR
- C) POWER SUPPLIED TO EACH RESISTOR
- D) TOTAL CURRENT FLOWING THROUGH THE BATTERY
- E) TOTAL POWER SUPPLIED BY THE BATTERY



ANSWERS: i) 4, 4, 4 A ; 60, 48, 128 V ; 240, 192, 512 W ; 4 A ; 944 W.

ii) 35, 308, 77 A ; 4620, 4620, 4620 V ; 161700, 1422960, 355740 W ; 420 A ; 1940400 W.

iii) 30, 20, 12, 12 A ; 240, 240, 144, 96 V ; 7200, 4800, 1728, 1152 W ; 62 A, 14880 W.

3. SUPER MAX! TANIA'S 1000 WATT HAIR DRYER OPERATES WITH A VOLTAGE OF 120V. CALCULATE THE DRYER'S CURRENT AND RESISTANCE. (8.33 A, 14.4  $\Omega$ )

4. AN ELEVATOR CARRIES 800 KG FROM GROUND LEVEL TO A HEIGHT OF 200m IN 10 MINUTES.


A) CALCULATE THE WORK DONE BY THE ELEVATOR.

RECALL:  $PE_0 + KE_0 \pm \text{Work} = PE + KE$  ( $1.6 \times 10^6 \text{ J}$ ) -

B) HOW MUCH POWER IS EXPENDED? (2667 WATTS)

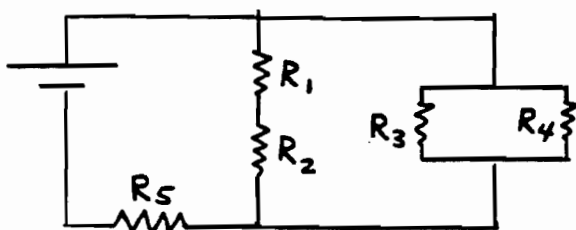C) IF THE MOTOR RUNS AT 240V AND IS 30% EFFICIENT, WHAT CURRENT DOES IT REQUIRE? (37A)

KIRCHHOFF'S LAW: INTUITIONS: FILL IN THE CHART.



GIVEN INFORMATION:


$$i_{\text{BATTERY}} = 20\text{A} \quad V_2 = 3\text{V}$$

$$i_1 = 2\text{A} \quad V_3 = 10\text{V}$$

$$i_4 = 4\text{A} \quad V_5 = 5\text{V}$$

	V	i	POWER	R
BATTERY				—
R <sub>1</sub>				
R <sub>2</sub>				
R <sub>3</sub>				
R <sub>4</sub>				
R <sub>5</sub>				

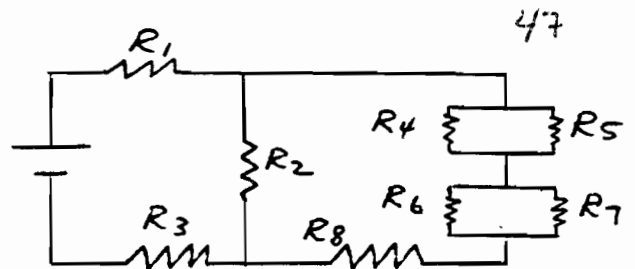
3. FOR THE CIRCUIT SHOWN, FILL IN THE UNKNOWN QUANTITIES IN THE CHART BELOW.



	BATTERY	1	2	3	4	5	6	7	8	
I					12 AMPS			15 AMPS		A
V	1250V								200V	V
R	-		$32 \Omega$			$45 \Omega$			$10 \Omega$	$\Omega$
P	56250 WATTS			12150 WATTS						W

4. TWO RESISTORS ARE COMBINED IN SERIES AND IN PARALLEL. THE MAXIMUM VALUE OF THE COMBINATION IS  $294 \Omega$ . THE MINIMUM IS  $36 \Omega$ . MAKE LIKE SHERLOCK 'OLMES AND DETERMINE THE VALUES OF THE INITIAL RESISTORS.  
( $42 \Omega$ ,  $252 \Omega$ )

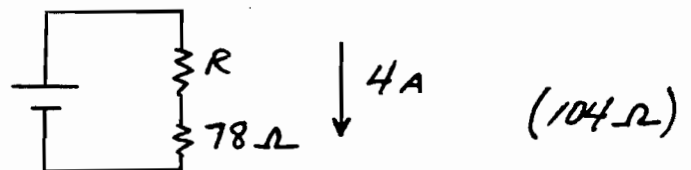5. INITIALLY, A RESISTOR HAS 7 AMPS FLOWING THROUGH IT. A  $78 \Omega$  RESISTOR IS NOW CONNECTED IN SERIES WITH THE FIRST. THE CURRENT FLOWING THROUGH THEM IS NOW ONLY 4 AMPS. FIND THE VALUE OF THE FIRST RESISTOR.



6. INITIALLY, A RESISTOR HAS 30 AMPS FLOWING THROUGH IT. A  $90 \Omega$  RESISTOR IS NOW CONNECTED IN PARALLEL WITH THE FIRST. THE TOTAL CURRENT SUPPLIED BY THE BATTERY IS NOW 36 AMPS. FIND THE VALUE OF THE INITIAL RESISTOR. ( $18 \Omega$ )

7. A 465 V BATTERY IS CONNECTED TO A  $12\ \Omega$  RESISTOR. THE RESISTOR RECEIVES 11532 WATTS OF POWER. FIND:

- CURRENT FLOWING THROUGH THE RESISTOR.
- INTERNAL RESISTANCE OF THE BATTERY.
- VOLTAGE DROP ACROSS EACH RESISTANCE.
- POWER DISSIPATED BY THE INTERNAL RESISTANCE OF THE BATTERY.
- PERCENT OF POWER WASTED BY THE INTERNAL RESISTANCE.


(31 A,  $3\ \Omega$ , 372 V, 93 V, 2883 W, 20%)

8. A 465 V BATTERY WHOSE INTERNAL RESISTANCE IS  $3\ \Omega$  IS CONNECTED TO A MOTOR WHOSE RESISTANCE IS ALSO  $3\ \Omega$ . FIND:


- CURRENT FLOWING AROUND THE CIRCUIT.
  - VOLTAGE DROP ACROSS EACH RESISTOR.
  - POWER DELIVERED TO EACH RESISTOR.
  - PERCENT OF POWER WASTED BY THE INTERNAL RESISTANCE.
- (77.5 A, 232.5 V, 18018.75 W, 50%)

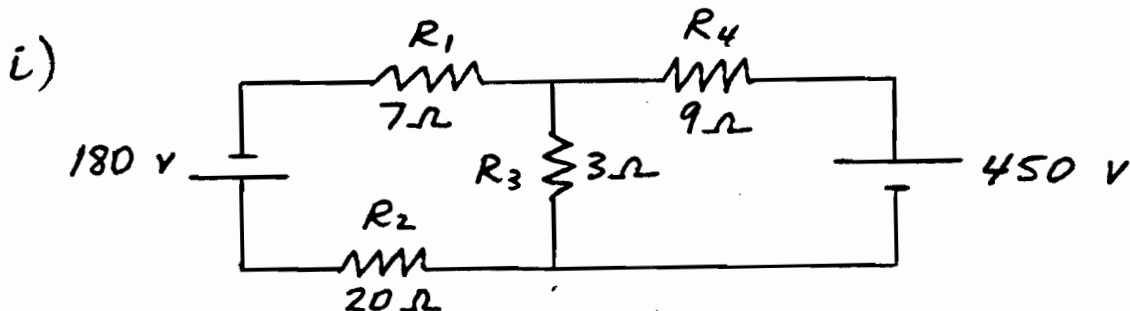9. FOR THE FOLLOWING CIRCUITS, FIND THE:

- CURRENT FLOWING THROUGH EACH RESISTOR AND THROUGH EACH BATTERY
- DROP IN VOLTAGE ACROSS EACH RESISTOR.
- POWER SUPPLIED TO EACH RESISTOR.
- POWER SUPPLIED BY EACH BATTERY.



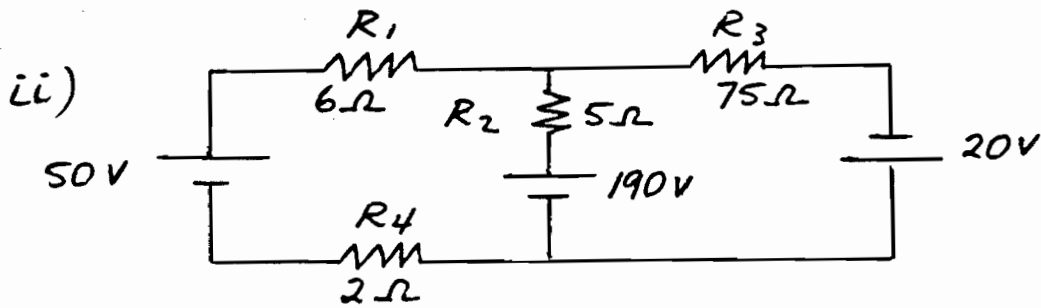(10, 10, 30, 40, 10, 40 A; 70, 200, 90, 360 V; 700, 2000, 2700, 14400 W; 1800, 18000 W)




(10, 12, 2, 10, -10, 12, 2 A; 60, 60, 150, 20 V; 600, 720, 300, 200 W; 500 W CHARGING BATTERY, 2280, 40 W)


10. THE AMMETER OF A WHEATSTONE BRIDGE CIRCUIT READS ZERO.

FIND THE VALUE OF THE UNKNOWN RESISTOR.

(1190 Ω)

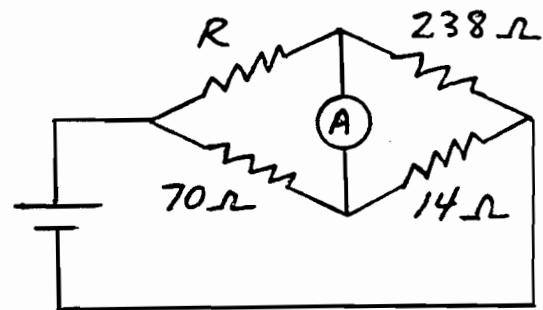

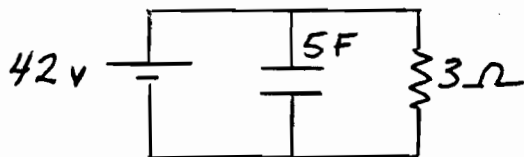11. THE CIRCUIT SHOWN BELOW IS PRESENTLY AT EQUILIBRIUM, THE CURRENT HAVING BEEN FLOWING FOR A VERY LONG TIME. FIND :




A) THE CHARGE AND THE ENERGY STORED IN THE CAPACITOR.

B) THE CURRENT FLOWING THROUGH THE RESISTOR AND THE POWER DELIVERED TO IT.

(210 C, 4410 J; 14 A, 588 W)

12.

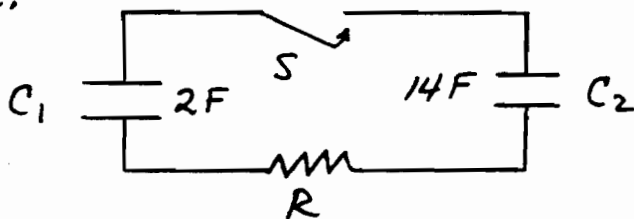


INITIALLY,  $C_2$  IS UNCHARGED, THE SWITCH IS OPEN AND  $C_1$  IS CHARGED TO A POTENTIAL OF 120 V.

A) FIND THE CHARGE AND ENERGY INITIALLY STORED IN  $C_1$ . (240 C, 14400 J)

B) THE SWITCH IS NOW CLOSED ALLOWING CHARGE TO FLOW FROM  $C_1$  TO  $C_2$  UNTIL THEIR VOLTAGES ARE EQUAL. AT THAT TIME, THE CIRCUIT IS IN EQUIL-

EQUILIBRIUM AND THE CHARGES STOP FLOWING, FIND THE :

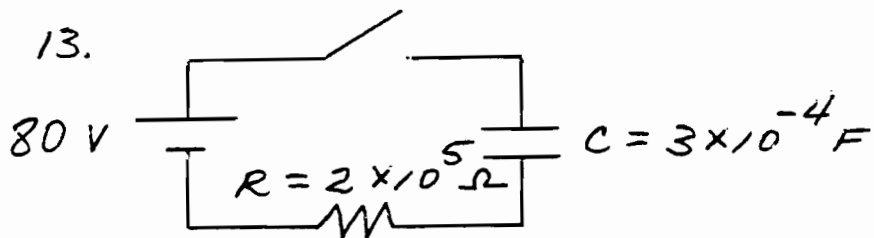
- i) CHARGE STORED BY EACH CAPACITOR (30 C, 20 C)
  - ii) VOLTAGE ACROSS EACH CAPACITOR (15 V, 15 V)
  - iii) ENERGY STORED BY EACH CAPACITOR (225 J, 157.5 J)
- c) FIND THE TOTAL ENERGY DISSIPATED BY THE RESISTOR WHILE THE CURRENT WAS FLOWING. (12600 J)



- A) FIND THE DECAY CONSTANT FOR THIS CIRCUIT.
  - B) AT  $t = 0$ , WE CLOSE THE SWITCH. FOR  $t = 15$  SECONDS, FIND THE :
    - i) CHARGE STORED IN THE CAPACITOR.
    - ii) CURRENT FLOWING THROUGH THE RESISTOR.
    - iii) DROP IN POTENTIAL ACROSS THE CAPACITOR.
    - iv) DROP IN POTENTIAL ACROSS THE RESISTOR.
- (60 SEC,  $5.31 \times 10^{-3} \text{ C}$ ,  $3.11 \times 10^{-4} \text{ A}$ , 17.3 V, 62.3 V)

14. FOR THE CIRCUIT IN PROBLEM 13,

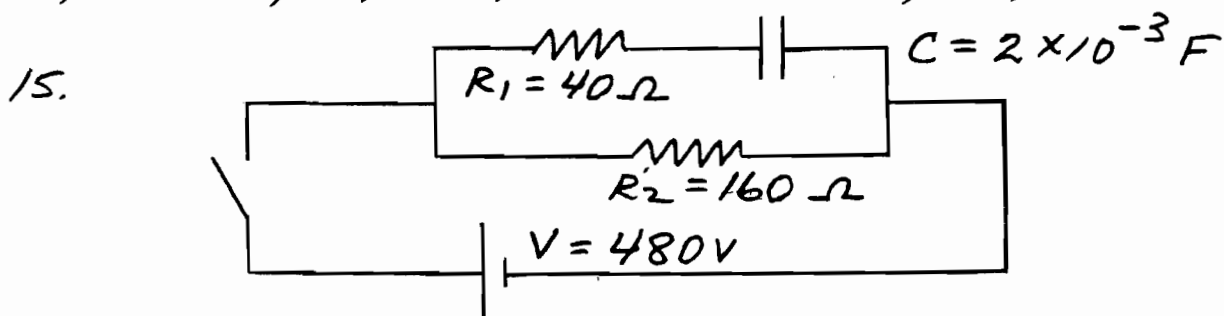
- A) AT  $t = 0$ , JUST AFTER CLOSING THE SWITCH, FIND THE CHARGE ON THE CAPACITOR, THE CURRENT, THE VOLTAGE ACROSS THE CAPACITOR AND THE VOLTAGE ACROSS THE RESISTOR.
  - B) AT  $t = \infty$ , FIND THE VALUES OF THE VARIABLES LISTED IN PART A.
- (0 C,  $4 \times 10^{-4} \text{ A}$ , 0 V, 80 V;  $2.4 \times 10^{-2} \text{ C}$ , 0 A, 80 V, 0 V)



AS WE CLOSE THE SWITCH, WE START OUR CHRONOMETER.

- AT  $t = 0$ , FIND THE CURRENT FLOWING THROUGH EACH RESISTOR.
- AT  $t = \infty$ , FIND THE CURRENT FLOWING THROUGH EACH RESISTOR AND THE CHARGE STORED BY THE CAPACITOR.
- AT  $t = .02$  SECONDS, FIND THE CHARGE STORED BY THE CAPACITOR, THE CURRENT FLOWING THROUGH EACH RESISTOR AND THE VOLTAGE DROPS ACROSS EACH DEVICE.

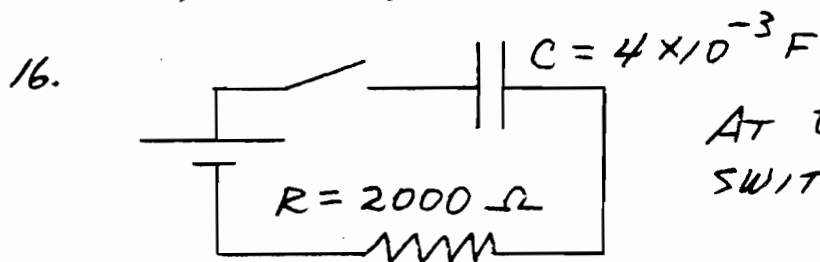(12 A, 3 A; 0 A, 3 A, .96 C; .21235 C, 9.3456 A, 3 A, 106.2 V, 373.8 V, 480 V)



AT  $t = 0$ , WE CLOSE THE SWITCH.

- FIND THE TIME FOR THE CURRENT TO DROP TO  $\frac{1}{e}$   $t_h$ , THAT IS 36.79%, OF ITS INITIAL VALUE.
- FIND THE TIME FOR THE CAPACITOR TO BECOME 90% FULL OF CHARGE,  
(8 SEC, 18.42 SEC)

17. REFER BACK TO PROBLEM 13 B. THE TIME IS

15 SECONDS AFTER CLOSING THE SWITCH. FIND THE:

- POWER DELIVERED TO THE CAPACITOR. ( $5.513 \times 10^{-3} \text{ W}$ )
- POWER DELIVERED TO THE RESISTOR. ( $1.941 \times 10^{-2} \text{ W}$ )
- POWER SUPPLIED BY THE BATTERY. ( $2.492 \times 10^{-2} \text{ W}$ )

